



NUST CHIP DESIGN CENTRE

Computer Architecture
Introduction to Processor Design

Lecture 1



Agenda

- From Transistors to Software
- Memory
- Pipelining
- Register File



Agenda


- **From Transistors to Software**
- Memory
- Pipelining
- Register File

Abstraction Layers

- Divide and conquer approach to designing complex digital systems!



Source: phys.org

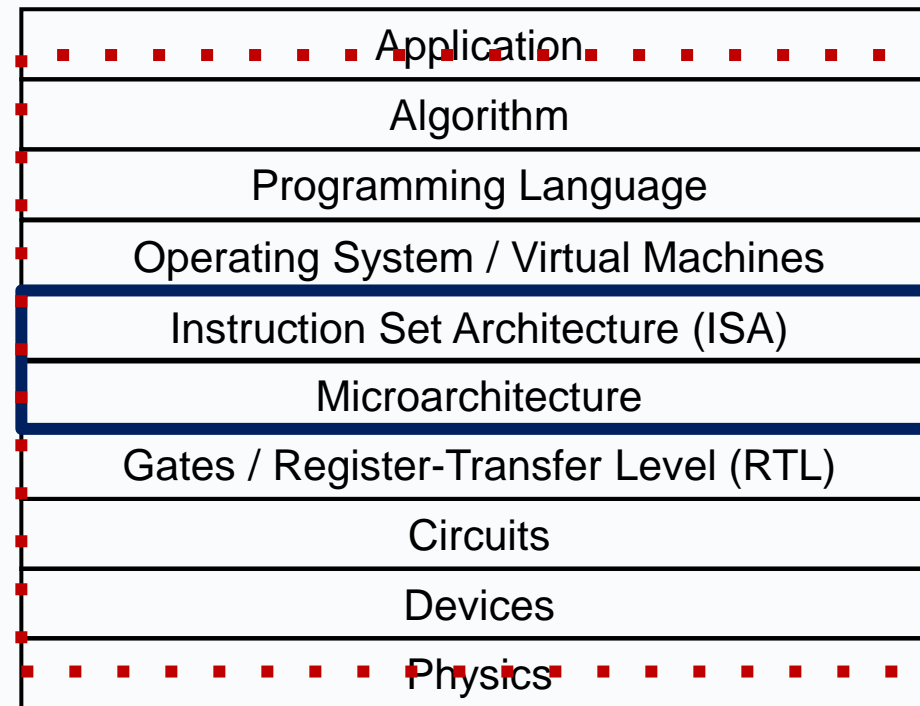


Classical view!

Modern view!


Computer Architecture is the science and art of designing computing platforms
 (hardware, interface, system SW, and programming model)

Transistor as a Switch

- MOSFET Transistors

 


n-type

 

p-type


Transistor as a Switch

- MOSFET Switching Behavior
 - n-type

 


Transistor as a Switch

- MOSFET Switching Behavior
 - n-type

 


Transistor as a Switch

- MOSFET Switching Behavior
 - p-type

 


Transistor as a Switch

- MOSFET Switching Behavior
 - p-type

 


Building Logic Gates

- Inverter or NOT Gate

 


Building Logic Gates

- Inverter or NOT Gate

 


Symbol

 


Building Logic Gates

- NAND Gate

 


Symbol

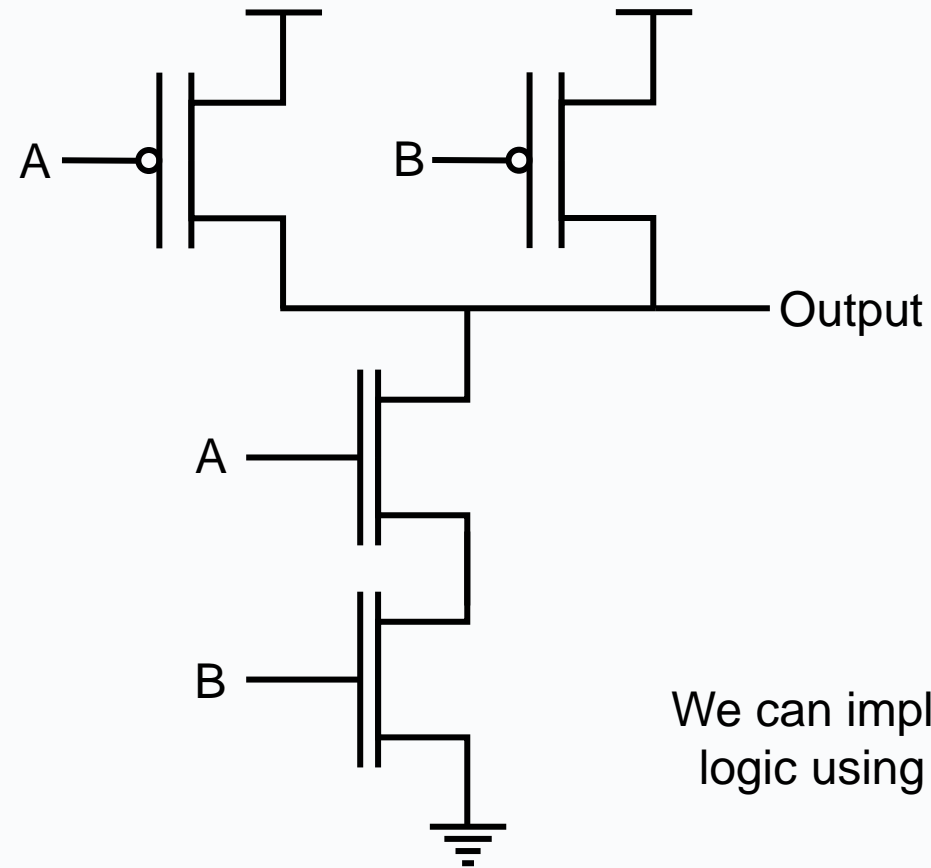

We can implement any Boolean logic using only NAND gates!


Building Logic Gates

- NAND (or NOR) Gate is universal gate

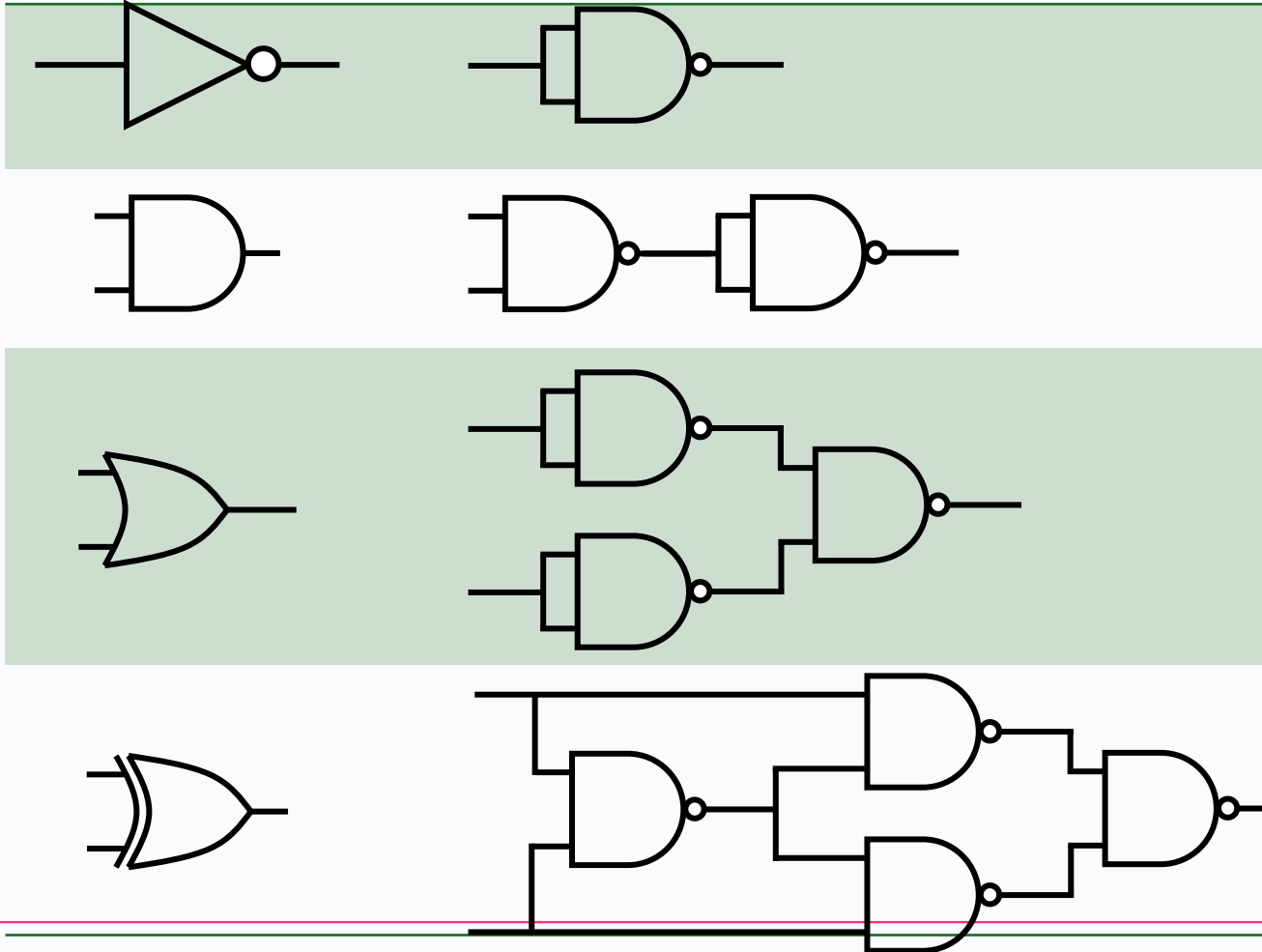


Combinational Logic

- What is this?

 

Two Input
Multiplexer!

 


SEL	OUT
0	IN1
1	IN2

Combinational Logic


- What is this?

Half Adder!

 Can we make a Full Adder
from two Half Adders?




 We can also implement
using only NAND Gates!




Sequential Logic

- Latch

 


CLK	D	Q
1	0	0
1	1	1
Else	x	Q

 


Sequential Logic

 
- Flip Flop / Register
 - Implemented using latches
 - There are other ways too ...



Multiple flip flops can be combined to store multiple bits!

CLK	D	Q
Rising	0	0
Rising	1	1
Else	x	Q

 


 

We have got all the ingredients to build a simple **ALU or even
a simple **Microprocessor** ...**

Building a Simple ALU

 
- Let's build an ALU with two operands and four operations!



**The operands can
be single bit or
multi-bit!**

From ALU to Microprocessor


- Let's add logic to select result

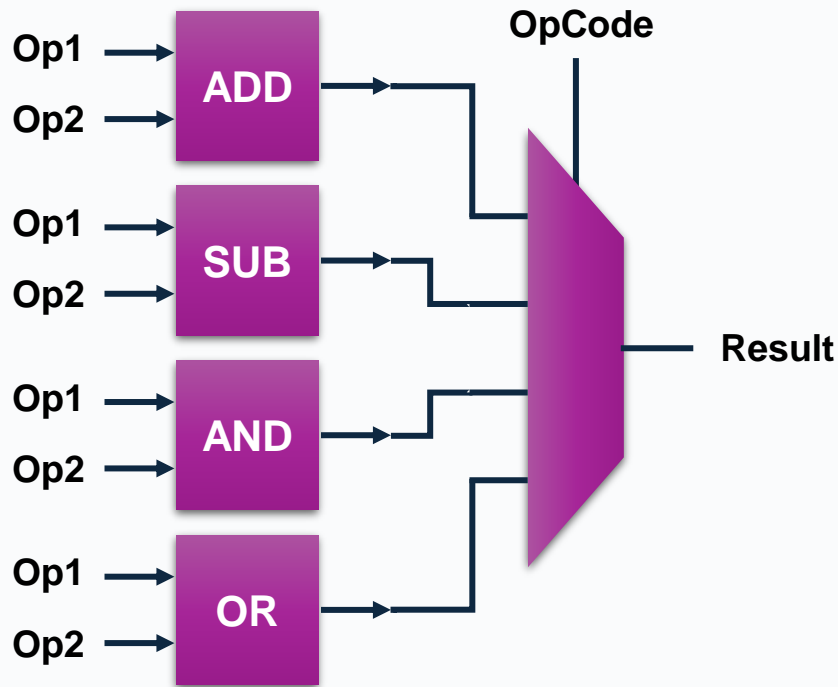

2-bit OpCode selects one of the four operations!

From ALU to Microprocessor

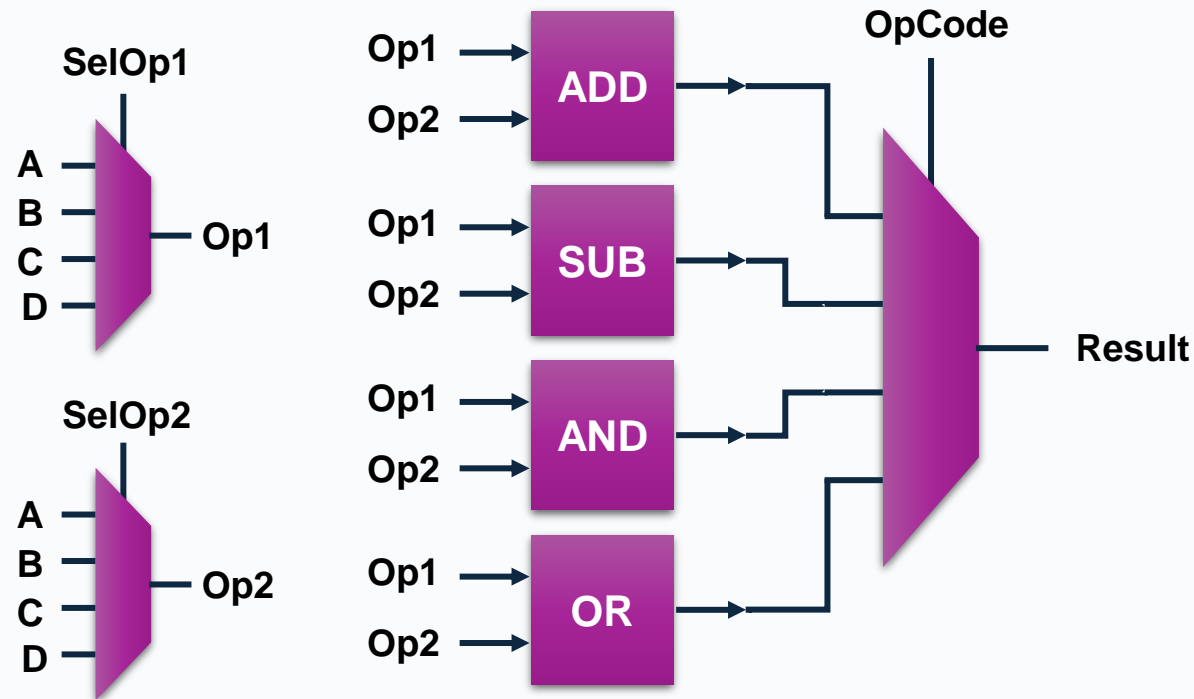
- Selecting two operands from four possible ones!



Together **SelOp1**, **SelOp2** and **OpCode** form **6 bits** that control the working of this simple Microprocessor!

A Simple Microprocessor

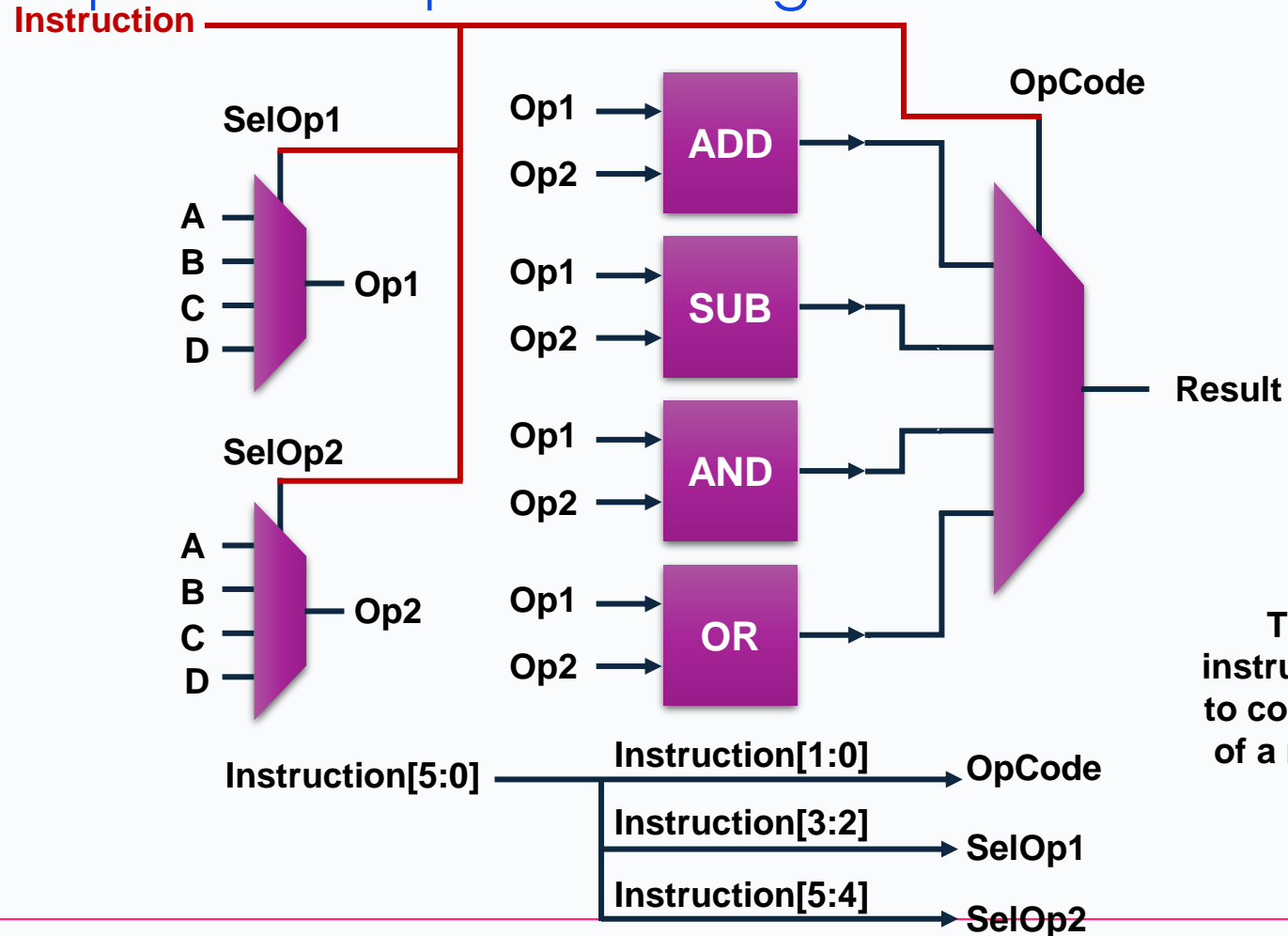- This Microprocessor operates using **6-bit Instruction!**



That's how the instruction is **decoded** to control the working of a microprocessor!

Programming Microprocessor

- To program simple microprocessor, we can use 6-bit instruction
 - Suppose we want to add B and C
 - OpCode = 00 for ADD
 - SelOp1 = 01 to select B
 - SelOp2 = 10 to select C
 - Corresponding Instruction is 100100 i.e., {SelOp2, SelOp1, OpCode}!
 - 100100 is **machine code** or **machine language**
 - That's the lowest level programming language understood directly by the hardware!
 - That's not quite readable or easier to use for humans, isn't it?
 - So, we use high-level languages!



Programming Microprocessor

- **ADD B, C** could be a possible syntax of assembly language instruction for our simple microprocessor!
 - Similarly, we can have **AND A, D**
 - **OR C, A** and so on ...
 - All the possible instructions form the **instruction set** for our microprocessor!

Programming Microprocessor

- High-level programming languages were made to simplify our task beyond assembly language!
 - For instance, a statement such **Result = A+B+C+D** in a high-level language may **replace** following assembly language instructions
 - ADD A, B # Store result in Result
 - MOV X, Result
 - ADD C, D
 - MOV Y, Result
 - ADD X, Y
 - We will need to add some more logic and temporary registers in our microprocessor to support all the above instructions!

Programming Microprocessor

- A **Compiler** translates software from a high-level language to assembly language!
 - There can be different assembly language codes for the same high-level language code!
- An **Assembler** translates the assembly language to machine language!
 - There is exactly one possible machine instruction for every assembly language instruction!
 - Compilers can directly generate machine code as well!
- **Microarchitecture** is the logic that executes the machine language!




Measuring Performance

- The implementation is simple!
 - Pure combinational circuit!
 - Output changes when input instruction changes!
- Performance
 - If we add a register at input (for instruction) and one at output (for result), each instruction takes one cycle to execute!
 - CPI (cycles per instruction) = 1
 - IPC (instructions per cycle) = 1

Measuring Performance

 
- How fast is this processor?
 - Depends on the critical path!
 - Critical path consists of
 - Two multiplexers
 - Subtractor (longest path in the ALU blocks!)
 - $$Max.Clock\ Rate = \frac{1}{2 \times (Multiplexer\ Delay) + Subtractor\ Delay + t_S + t_{CLK2Q}}$$





Agenda

 
- From Transistors to Software
- **Memory**
- Pipelining
- Register File



Let's add **memory** for multiple instructions ...

Adding Instruction Memory

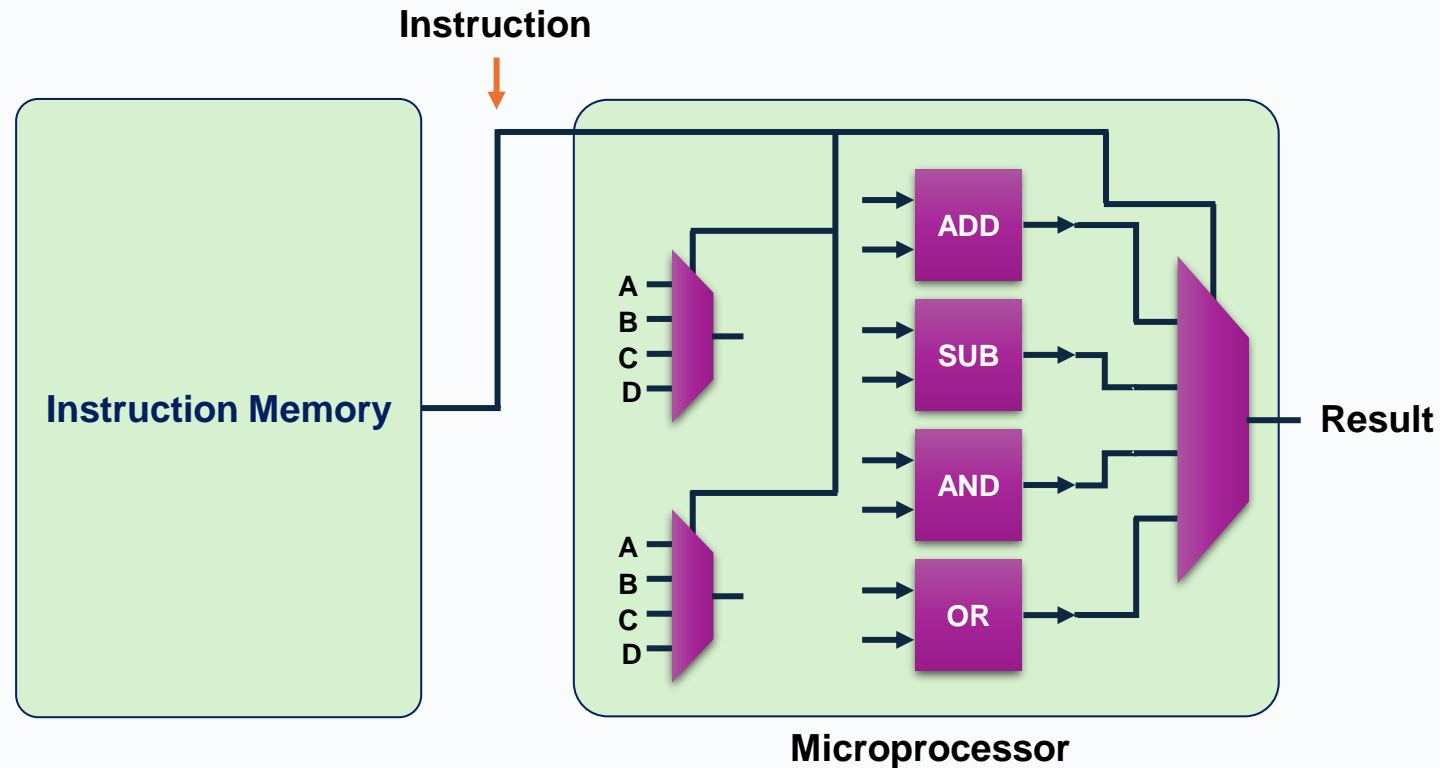- **Instruction Memory** can hold multiple instruction!




Adding Instruction Memory

- 6-bit Instructions require a simple memory where each location may be 6-bit
 - Practical memories are sized in bytes (8 bits) and usually an address corresponds to a byte address!
- Let's add an instruction memory of size 8x6 bits
 - 8 locations
 - Each location is 6 bits in size!
 - How many bits do we need for address?
 - 3 bits
 - Instruction Cache is addressed using “Program Counter”
 - Also called “Instruction Pointer Register”!
 - Usually a *register* in actual microprocessors!


Program Counter / Instruction Pointer

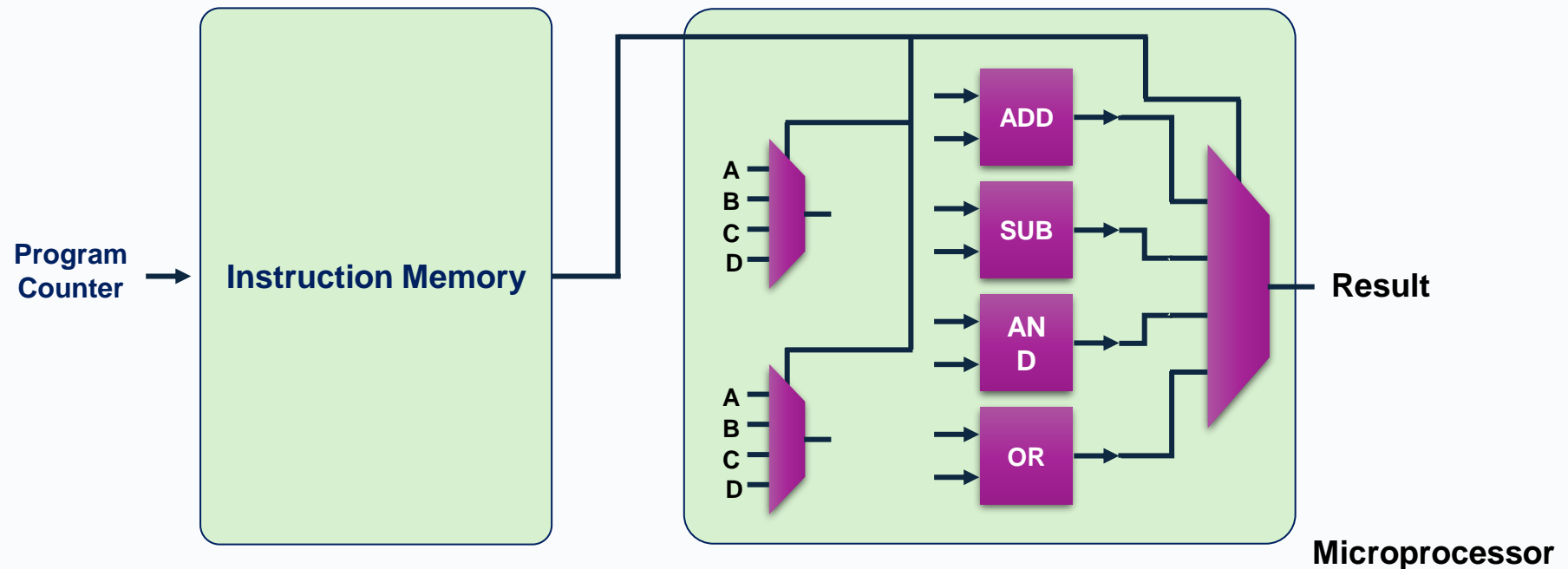- Program Counter (PC)
 - To address instruction cache!
 - For 8x6 bit instruction cache, PC is 3-bit!
 - PC can go from 000 to 111 to select 8 instructions!




Executing Multiple Instructions

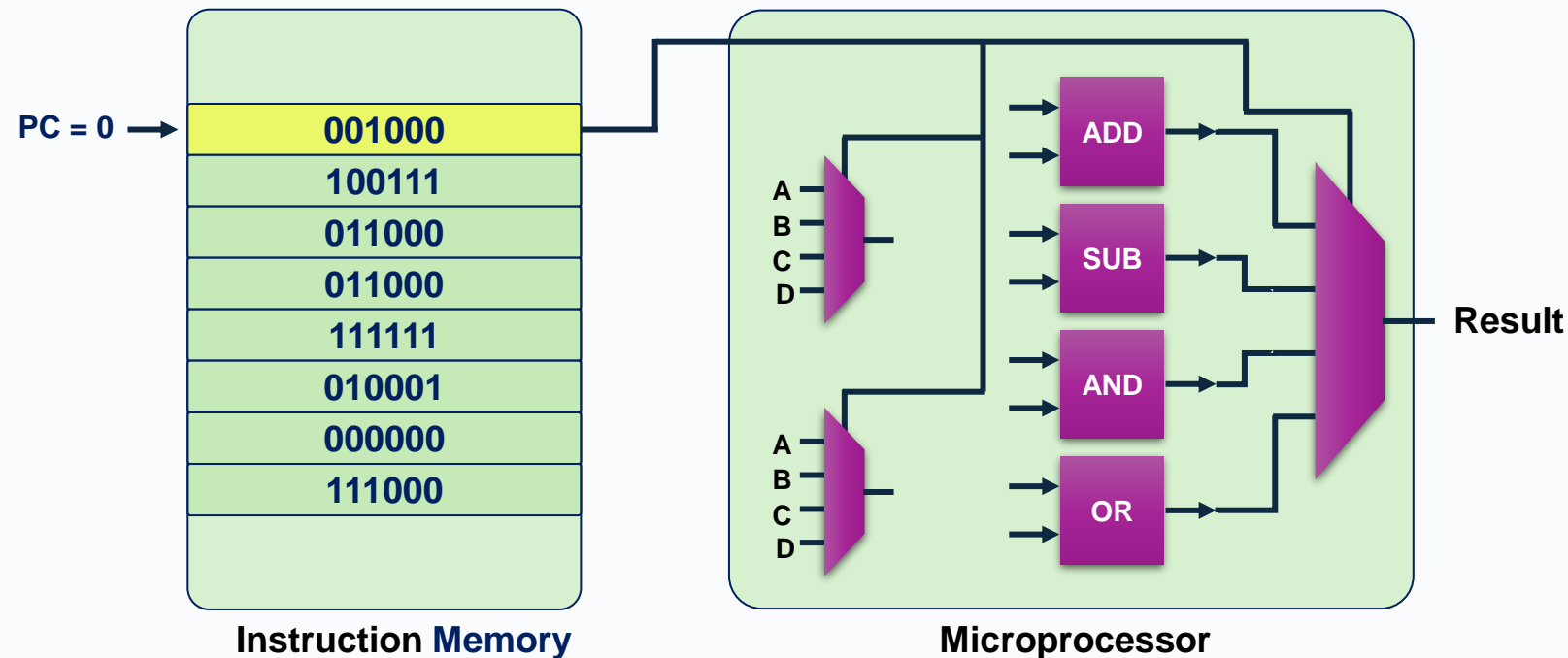- PC is incremented to select successive instructions!




Executing Multiple Instructions

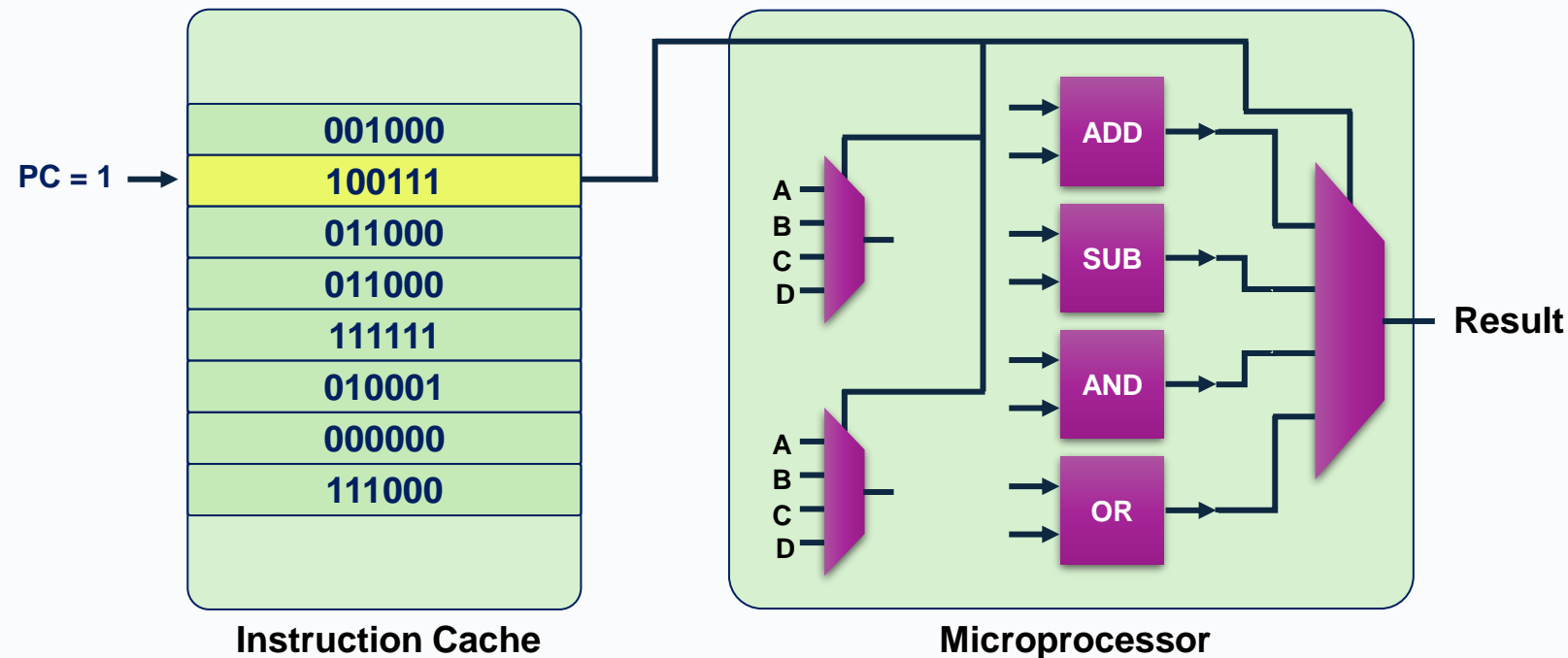
- PC is incremented to select successive instructions!



Executing Multiple Instructions

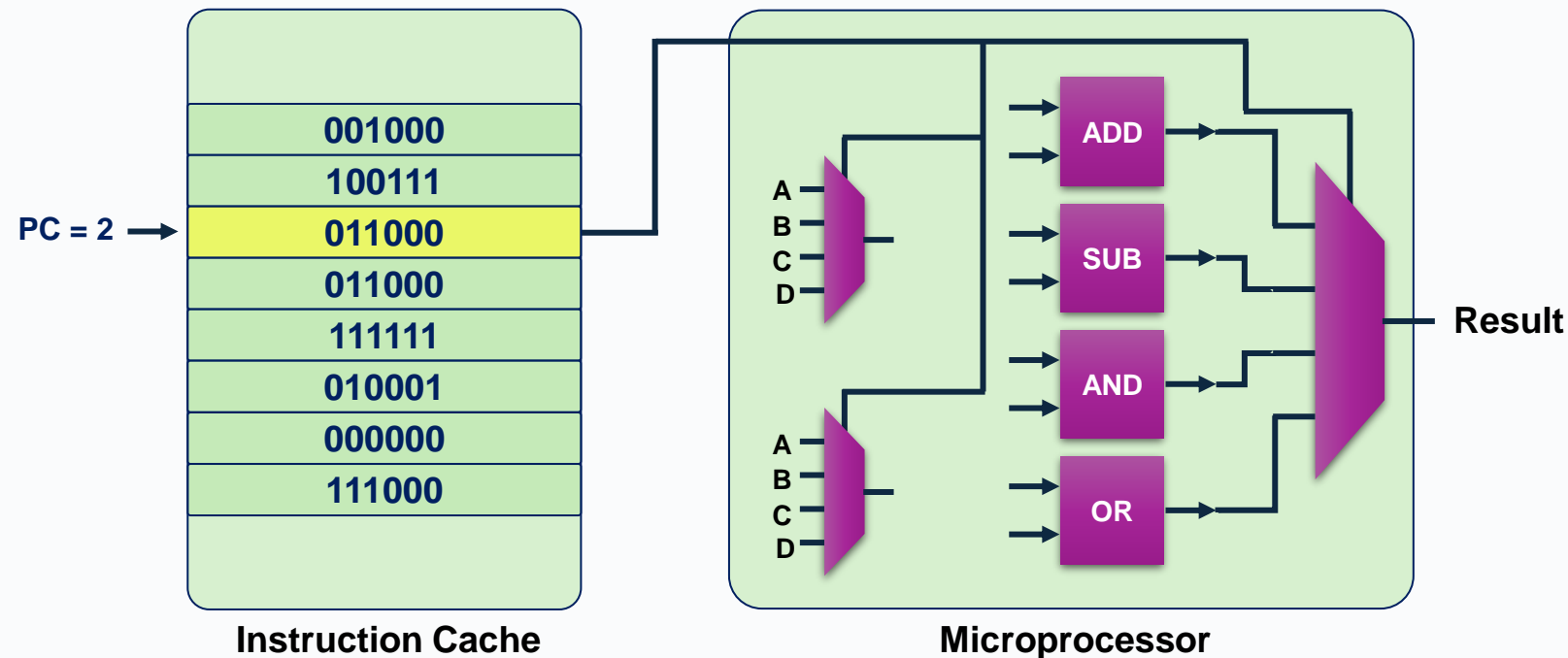- PC is incremented to select successive instructions!




 

Just like **Instruction Memory, we have **Data Memory**
to hold operands to be processed...**


Adding Data Memory

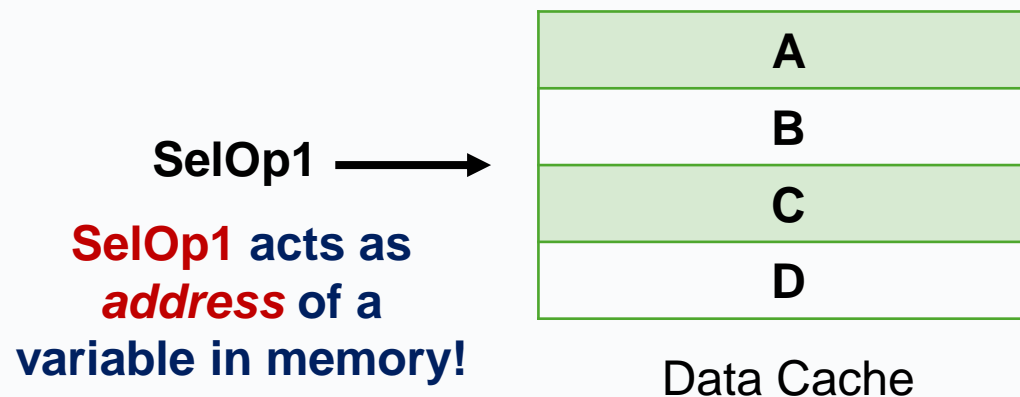- Can add two simple data memories to load operands! (multiplexers will be removed)
 - Each data memory can be $(4 \times n)$ bits
 - 4 locations
 - Each having an n -bit operand!
 - 2-bit address to select one of the four operands!




Usually, microprocessors load one operand at a time from memory instead of two!

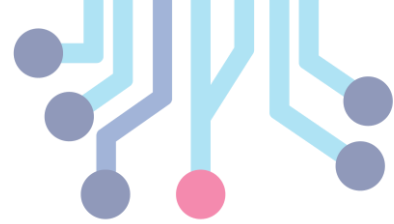Operands are loaded into registers inside CPU!



 It is also possible to have a single memory for instructions as well as data!




With one memory for I or D, instruction is loaded in a different clock cycle while data is accessed in a different cycle!




Agenda

 - From Transistors to Software
- Memory
- **Pipelining**
- Register File




 Can we **improve** our processor's **performance**?



Pipelining is an important technique for improving performance ...

A Laundry Analogy

 


- Pipelining helps execute multiple tasks in parallel
- Improves throughput ...

Source: Computer Organization and Design (RISC-V Edition), Patterson and Hennessy


Pipelining Processor

- Without Pipelining

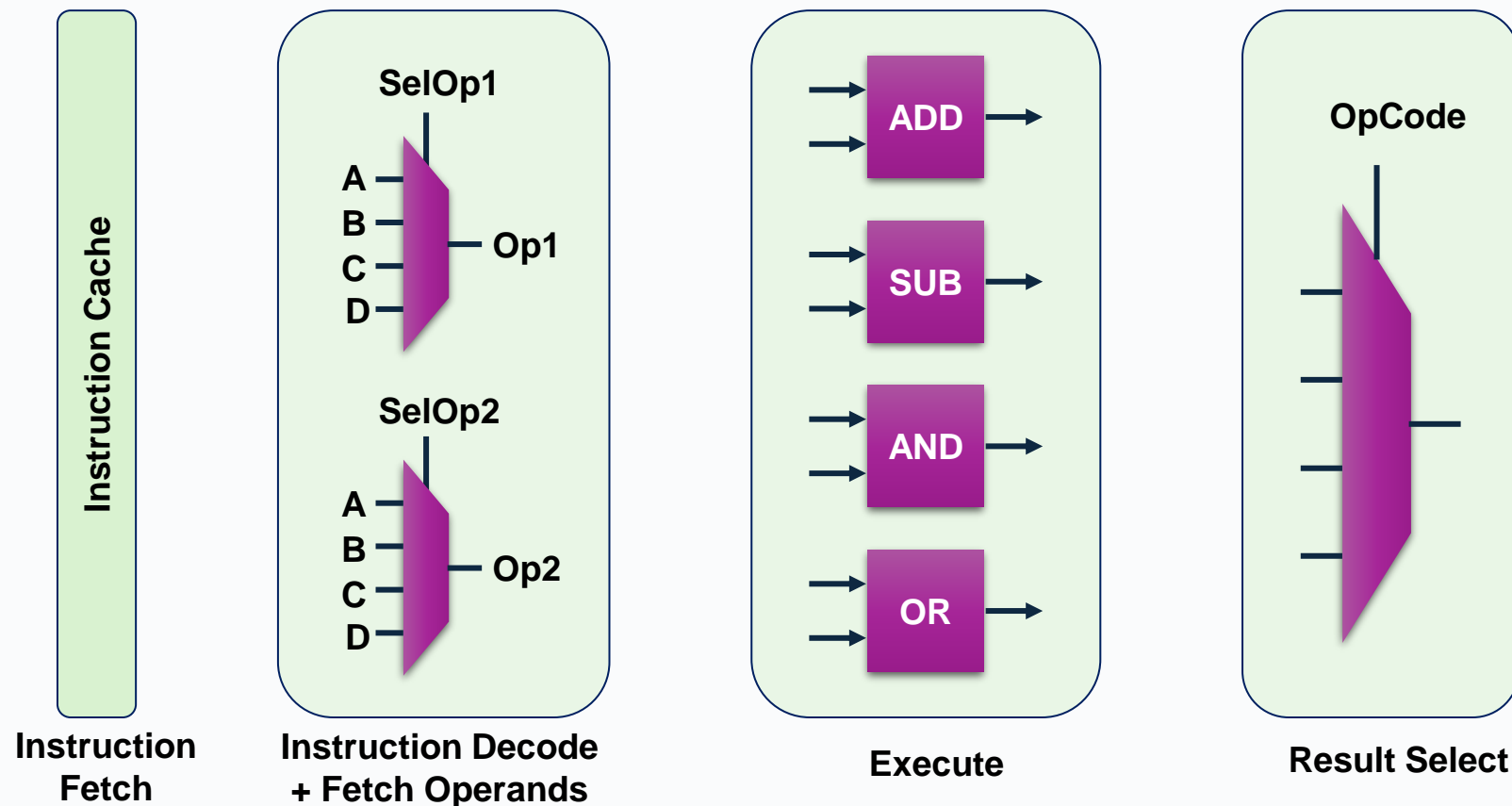


Pipelining Processor


- Adding Pipeline Registers

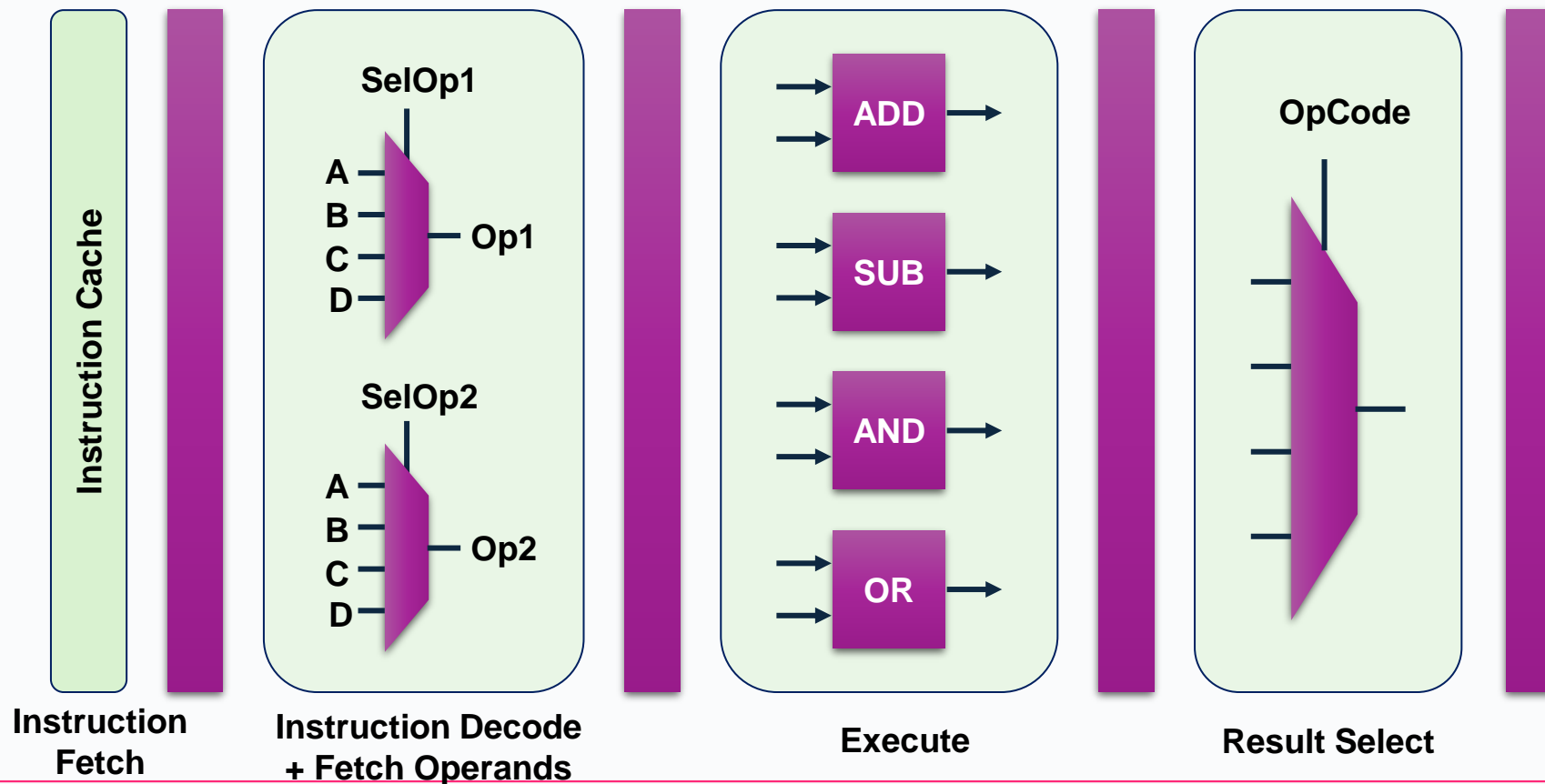

Pipelining Processor

- Register Sizes

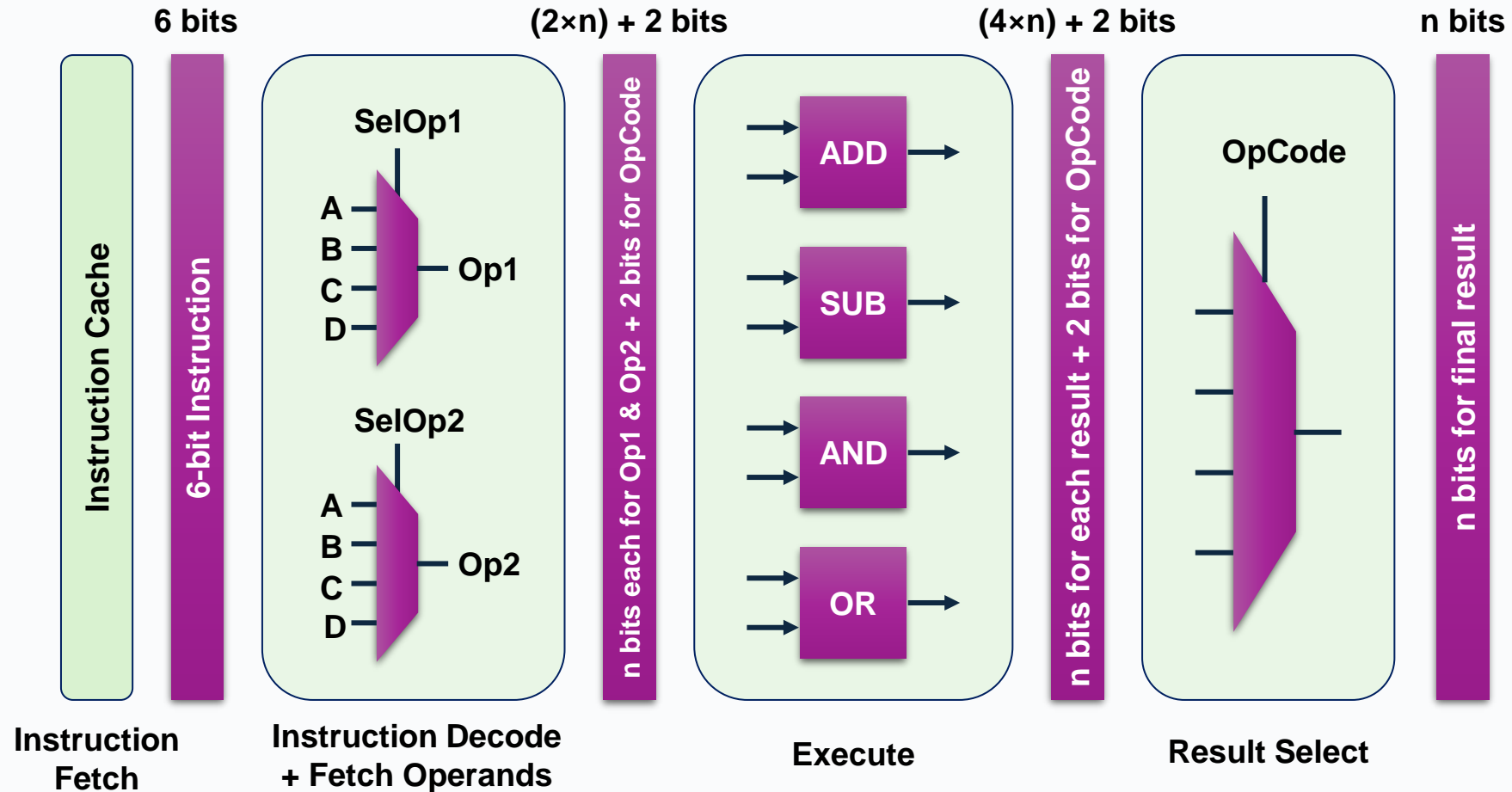

 

What's the **critical path in pipelined implementation?**


Critical Path in Pipelined Design

- It's reduced to that of subtractor
 - Assuming subtractor path is longer than that of multiplexer!
 - $Max\ Clock = \frac{1}{Subtractor\ Delay + t_S + t_{CLK2Q}}$
 - Much faster than the previous design!
 - As first instruction result (OpCode+Operands) goes to second pipelined register
 - A new instruction can be loaded from instruction cache to the first pipelined register!




Agenda

 - From Transistors to Software
- Memory
- Pipelining
- **Register File**



 In load-store architectures (all recent ones), data is **loaded into registers inside CPU, which act as temporary storage, and after processing it is **stored** back in data memory...**



Let's add a **Register File** to our processor and modify the instruction set a bit ...


Architecture with Register File


- Let's assume there are four n-bit registers in processor named x0, x1, x2 and x3!
 - Let's assume x0 is hardwired to 0 value!
 - Two instruction bits select source operand 1 (**rs1**)
 - Two instruction bits select source operand 2 (**rs2**)
 - Two instruction bits select destination operand (**rd**) where the result from ALU is stored!
- Our instruction is now 8-bit!
 - Instruction[1:0] → opcode
 - Instruction [3:2] → rs1
 - Instruction [5:4] → rs2
 - Instruction [7:6] → rd

Architecture with Register File

- Example
 - `add x2, x1, x3`
 - opcode = 00
 - rs1 = 01
 - rs2 = 11
 - rd = 10
 - Instruction = {10 11 01 00}
- Similarly, we can have sub, and, or etc.


Microarchitecture with Register File

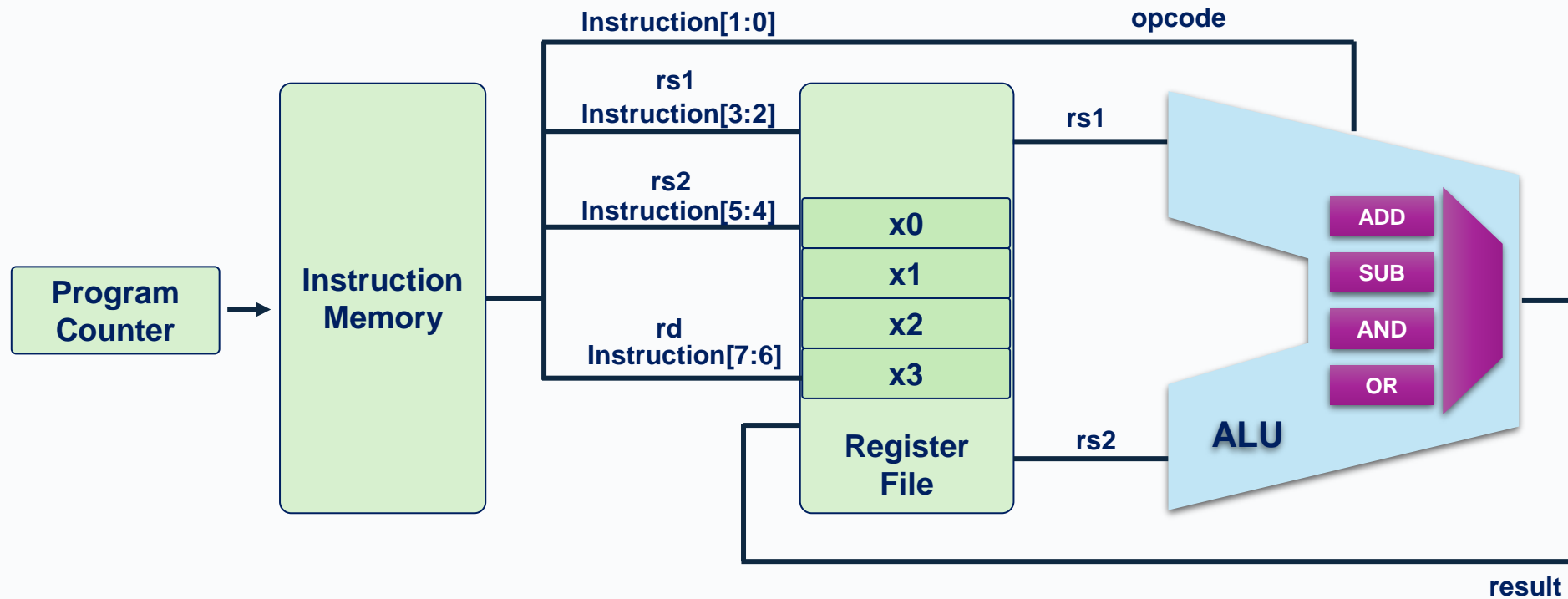

 

**We will see how more complex processors are build
based on same **fundamental** principles!**

Main Components in a Processor

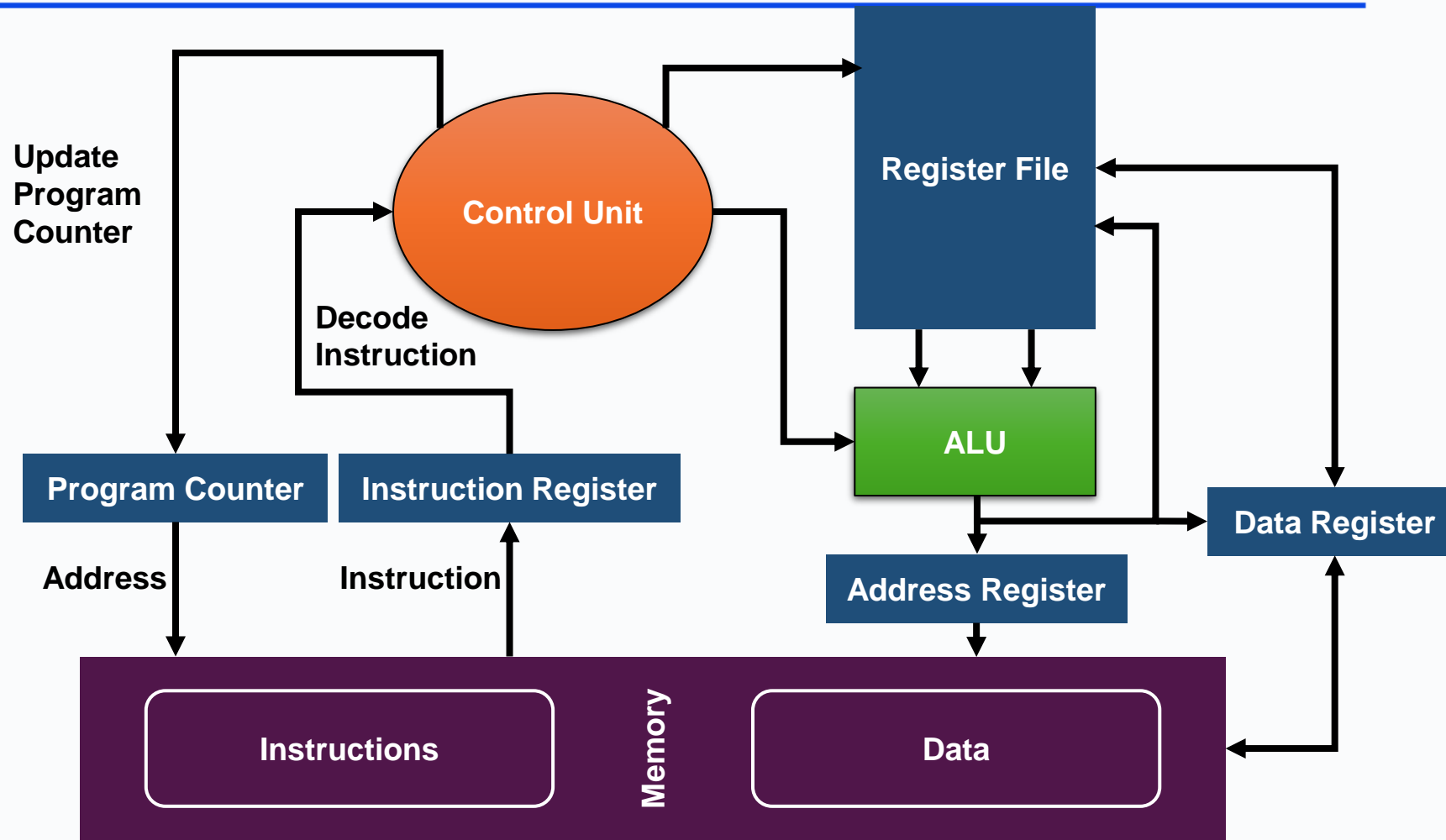

Thank You



NCDC | NUST
CHIP
DESIGN
CENTRE