



---

NUST CHIP DESIGN CENTRE

# **Digital Logic Design**


## Timing in Sequential Circuits

 
# Sequential Networks

---




Timing: Setup Time and Hold Time Constraints




 

# Sequential Networks

 

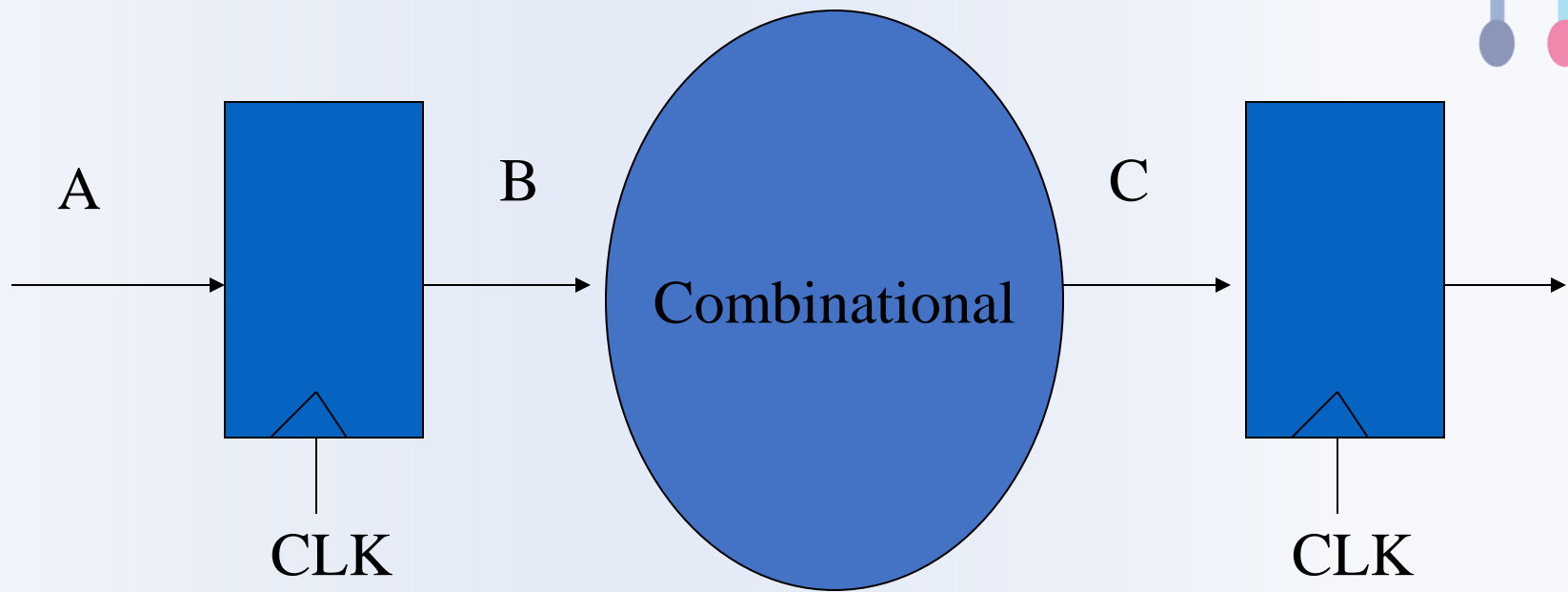A typical sequential network has both a combinational circuit and flip-flops.



$$t_{cq} + t_{comb} + t_{setup} \leq T$$

Clock period


$$t_{hold} < t_{cq} + t_{comb}$$

Shortest path
 
# Input Timing Constraints




- Setup time:  $t_{\text{setup}}$  = time *before* the clock edge that data must be stable (i.e. not changing)
- Hold time:  $t_{\text{hold}}$  = time *after* the clock edge that data must be stable
- Aperture time:  $t_a$  = time around clock edge that data must be stable ( $t_a = t_{\text{setup}} + t_{\text{hold}}$ )





 
# Output Timing Constraints


- Propagation delay:  $t_{pcq}$  = time after clock edge that the output  $Q$  is guaranteed to be stable (i.e., to stop changing)
- Contamination delay:  $t_{ccq}$  = time after clock edge that  $Q$  might be unstable (i.e., start changing)




 
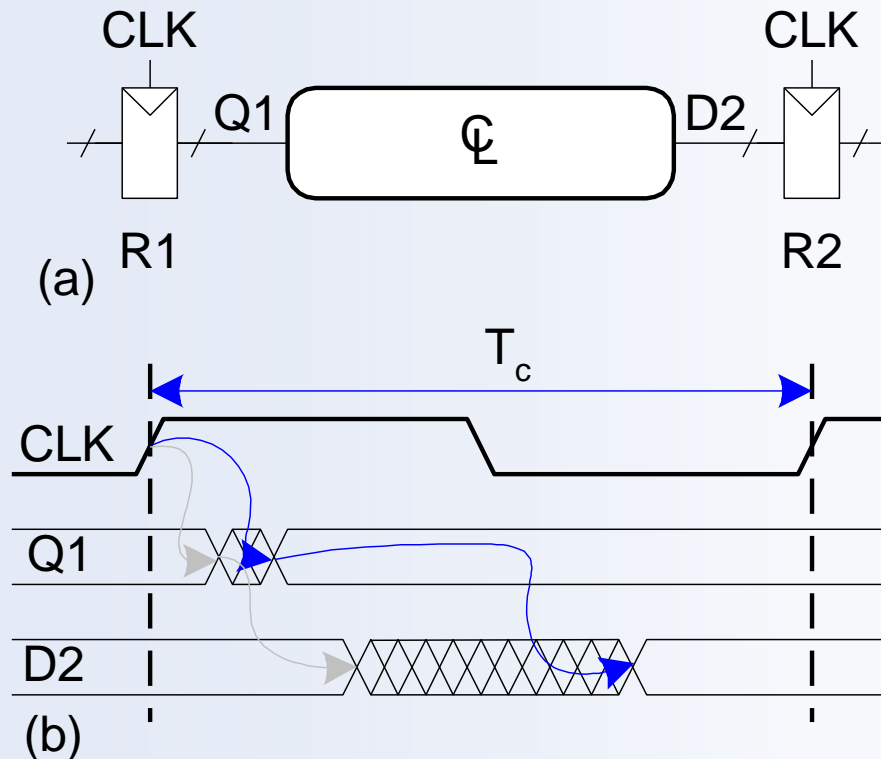
# Dynamic Discipline


- The delay between registers has a **minimum** and **maximum** delay, dependent on the delays of the circuit elements



 
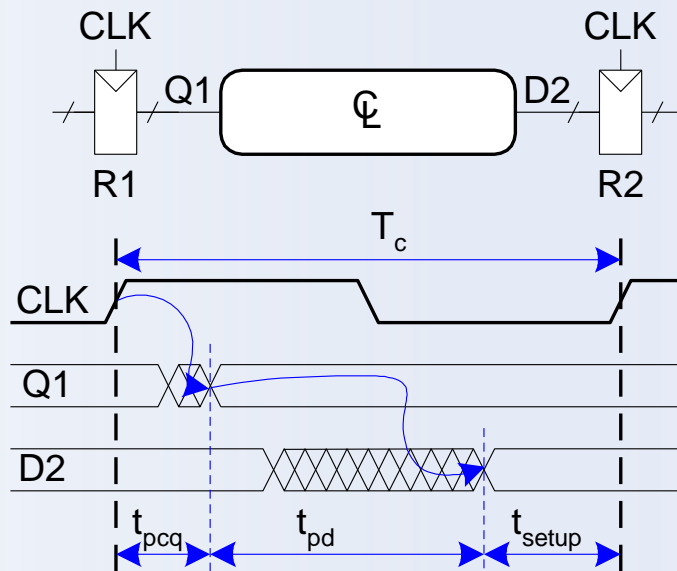
# Setup Time Constraint


- The setup time constraint depends on the **maximum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least  $t_{\text{setup}}$  before the clock edge.



$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$

 
$$t_{pd} \leq T_c - (t_{pcq} + t_{\text{setup}})$$




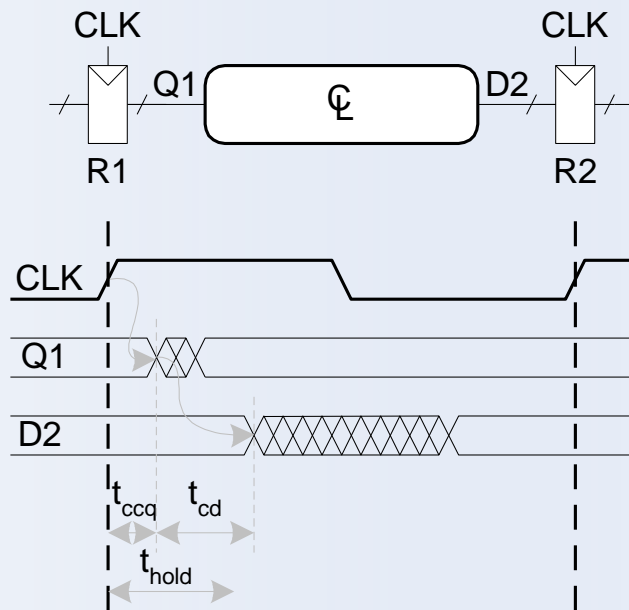
# Hold Time Constraint


- The hold time constraint depends on the **minimum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least  $t_{\text{hold}}$  after the clock edge.



$$t_{\text{hold}} < t_{\text{ccq}} + t_{\text{cd}}$$

$$t_{\text{cd}} > t_{\text{hold}} - t_{\text{ccq}}$$

## A decorative graphic consisting of stylized circuit lines and nodes. The lines are light blue and the nodes are dark blue, with one central node being pink. The design is symmetrical and modern.

 
$$t_{pd} =$$
$$t_{cd} =$$

## Setup time constraint:

$$T_c \geq$$

$$f_c = 1/T_c =$$

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

Hold time constraint:

$$t_{ccq} + t_{pd} > t_{hold} ?$$

# Timing Analysis



## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$


$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

Hold time constraint:


$$t_{ccq} + t_{pd} > t_{\text{hold}} ?$$

$$(30 + 25) \text{ ps} > 70 \text{ ps} ? \text{ No!}$$

# Fixing Hold Time Violation



Add buffers to the short paths:

 

$$t_{pd} =$$

$$t_{cd} =$$

Setup time constraint:

$$T_c \geq$$

$$f_c =$$

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$


Hold time constraint:

$$t_{ccq} + t_{pd} > t_{\text{hold}} ?$$



# Fixing Hold Time Violation

Add buffers to the short paths:

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

Hold time constraint:


$$t_{ccq} + t_{pd} > t_{\text{hold}} ?$$

$$(30 + 50) \text{ ps} > 70 \text{ ps} ? \text{ Yes!}$$


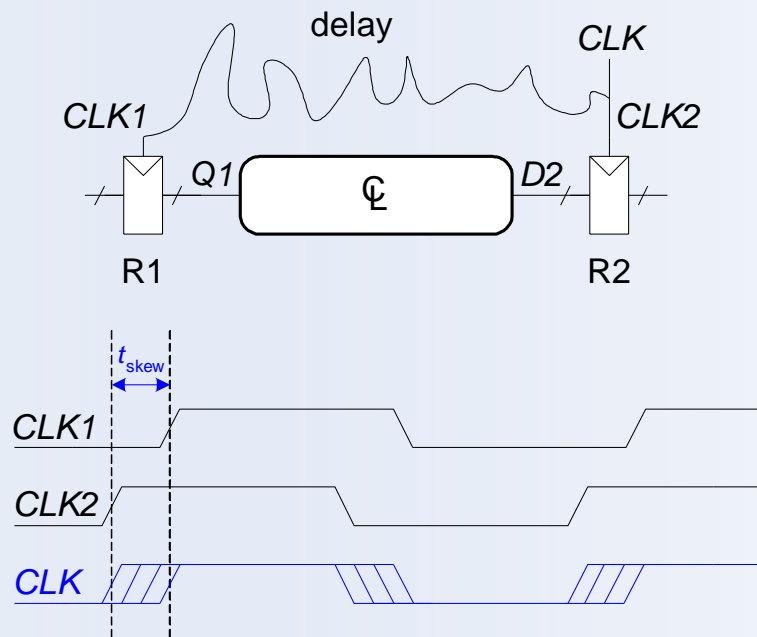
# Clock Skew


- The clock doesn't arrive at all registers at the same time
- Skew is the difference between two clock edges
- Examine the worst case to guarantee that the dynamic discipline is not violated for any register – many registers in a system!


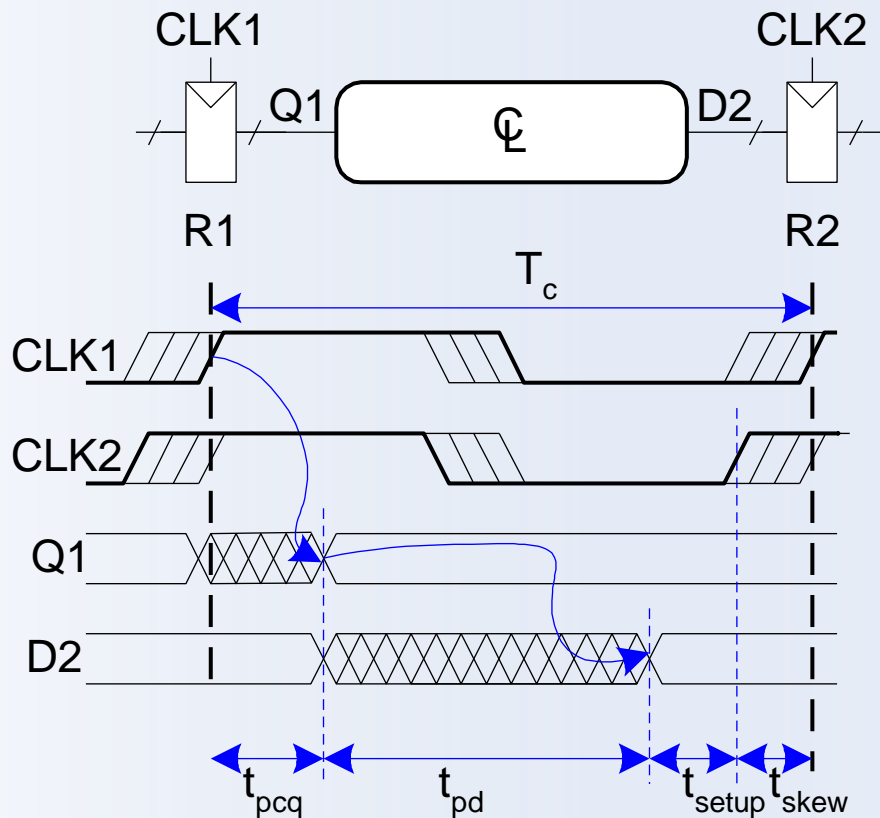
# Setup Time Constraint with Clock Skew



- In the worst case, the CLK2 is earlier than CLK1




$$T_c \geq t_{pcq} + t_{pd} + t_{setup} + t_{skew}$$
$$t_{pd} \leq T_c - (t_{pcq} + t_{setup} + t_{skew})$$
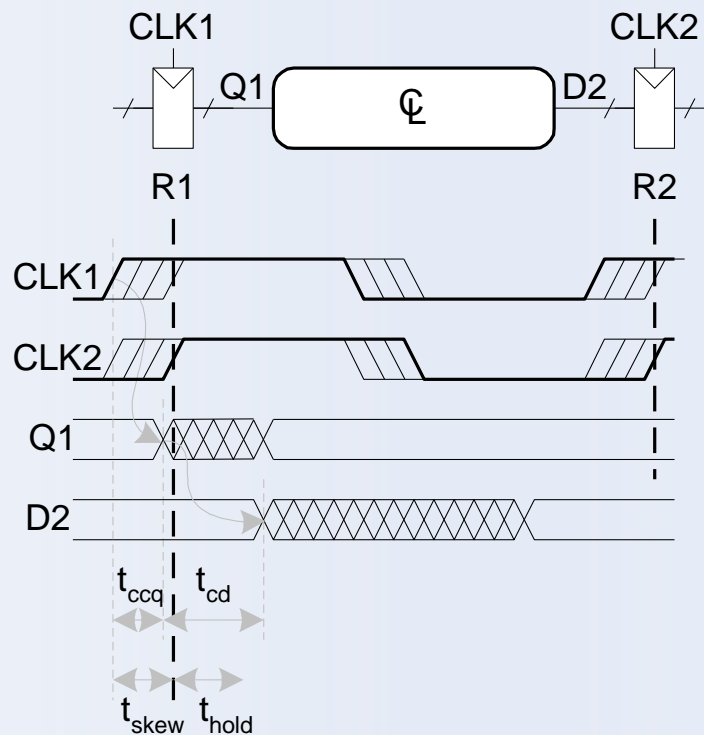
# Hold Time Constraint with Clock Skew



- In the worst case, CLK2 is later than CLK1



$$t_{ccq} + t_{cd} > t_{hold} + t_{skew}$$

$$t_{cd} > t_{hold} + t_{skew} - t_{ccq}$$



# Timing and Retiming

---



- Retiming: Adjust the clock skew so that the clock period can be reduced.
- Add a few more examples on timing and retiming.

# Fixing Setup Time Violation

---



1. Increase clock period
2. Optimize datapath
  - a. Pipeline
  - b. Logic optimization
  - c. Buffer removal
  - d. Routing optimization
3. Use faster cells
4. Relax constraints for non-critical paths

# Fixing Hold Time Violations

---



1. Add delay to datapath
  - a. Insert buffers
  - b. Interconnect delay
2. Reduce clock skew
  - a. Clock tree optimization
3. Increase hold time requirements
  - a. Use of retiming buffers
    - i. Retiming involves repositioning registers in the circuit to balance the timing constraints. By shifting flip-flops, it's possible to meet the required hold time without impacting overall circuit performance.
  - b. Insert hold buffers
4. Adjust operating conditions
  - a. Lowering voltage
  - b. Temperature adjustment
5. Change Flip-flop type